

COEN 6501 Digital design and Synthesis

Oct. 18, 2010

Lecturer: Asim J. Al-Khalili

Answer all Questions. All Questions carry equal marks

Exam Duration: 1hr 30 min.

No books, papers or calculators are allowed.

Question 1

Design a circuit to give F

$F = X^3$ where X is a 2-bit unsigned binary number, ie $X = x_1 x_0$

- Use Truth Table
- Use carry Save Adders

Question 2

- Using Booth Algorithm multiply $A = -23$ and $B = 6$.
- Using a 3 to 8 decoder map (recode) the 3 bits of the multiplicand according to the following equation:

$$Z_i = -2x_{i+1} + x_i + x_{i-1}$$

(ie 3 bit input $-2x_{i+1}, x_i, x_{i-1}$ giving 5 bit output $+, -, 0, 1, 2$)

Question 3


- Use Carry Select adder to implement optimally the addition of two 21 bit unsigned numbers.
- How does that compare with Manchester Carry Adder of the same size ? Calculate the delay and area in terms of Half Adders, Full adders, gates and Muxes.

Q1 $F = x^3$



a) Using Truth Table max value of $F = (11)^3 = 27$

| x_1, x_0 | M_4 | M_3 | M_2 | M_1 | M_0 |
|------------|-------|-------|-------|-------|-------|
| 0 0 | 0 | 0 | 0 | 0 | 0 |
| 0 1 | 0 | 0 | 0 | 0 | 1 |
| 1 0 | 0 | 1 | 0 | 0 | 0 |
| 1 1 | 1 | 1 | | 1 | 1 |

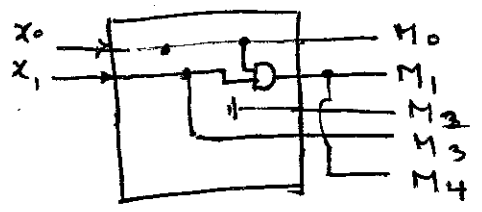- $M_0 = x_0$
- $M_1 = x_1 x_0$
- $M_2 = 0$
- $M_3 = x_1$
- $M_4 = x_1 x_0$



b) Using CSA method

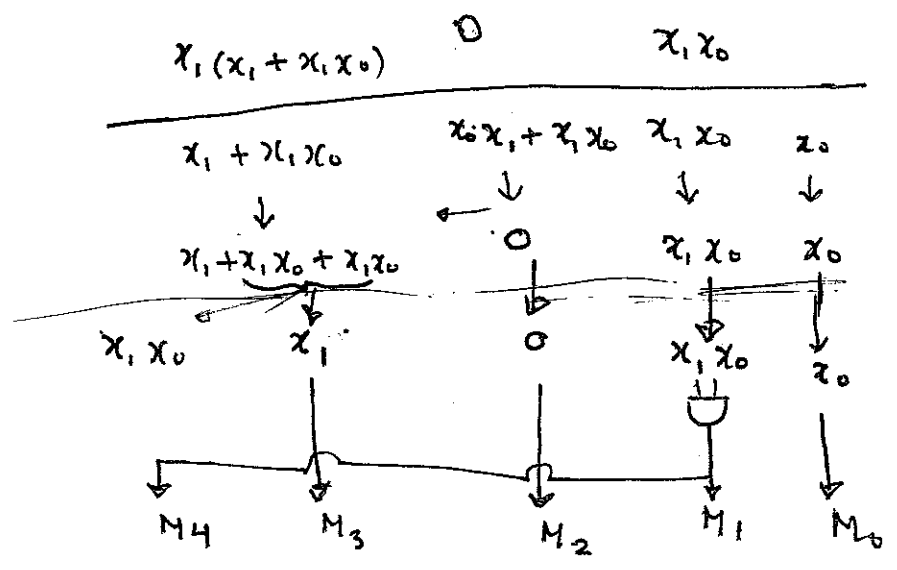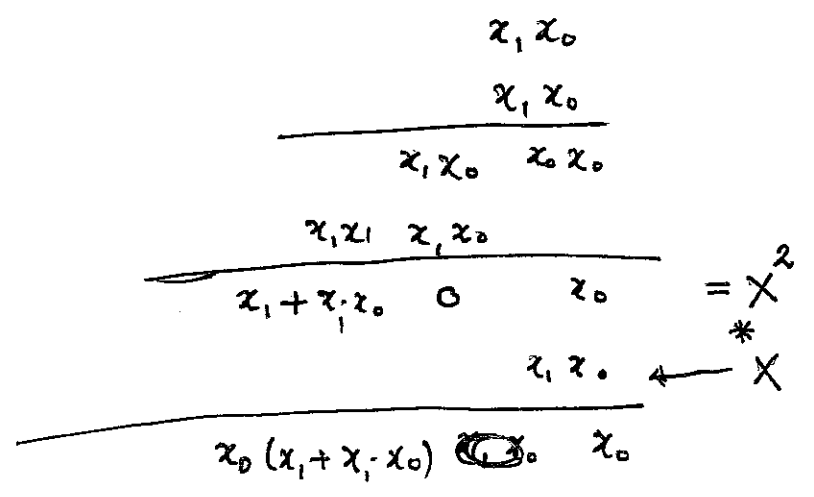

Q2

$A = (-23)_{10}$

$A = 0010111$

$-A = 1101001$

$B = 0000110$

$A * B$

=

$$\begin{array}{r} 11101001 \\ 00001100 \\ \hline 11101001 \\ 00001100 \\ \hline 11101110110 \end{array}$$

Code (0 2 -2)

Then $A * B =$


$$\begin{array}{r} 11101001 * \\ 0 \quad 2 \quad -2 \\ \hline 0000101110 \\ 11010010 \\ \hline 11101110110 \end{array}$$

$A * B$ is a -ve number taking its complement gives

$00010001010_2 \text{ or } -138_{10}$

b)



$Z_i = -2x_{i+1} + x_i + x_{i-1}$

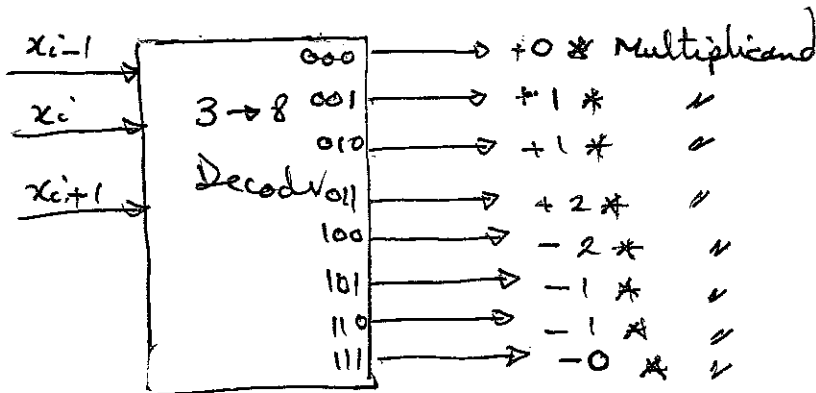

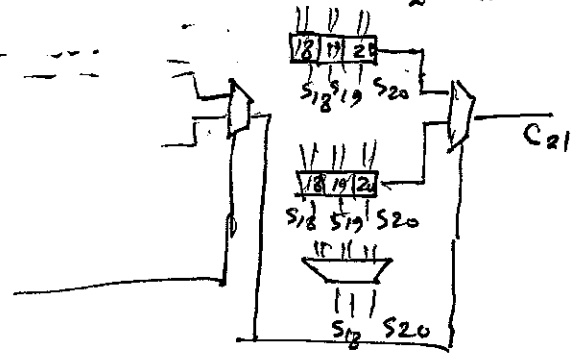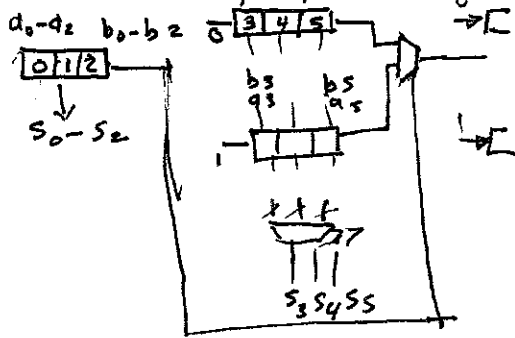Q3 → Carry Select



Various options of implementation is possible, here are some possibilities

- 2 * 2 * 2 * 2 * 2 * 2 * 2 * 2 * 2 * 3 — $3 + 7 * \frac{1}{2} = 6 \frac{1}{2} \tau_{FA}$
- 3 * 3 * 3 * 3 * 3 * 3 * 3 — $3 \tau_{FA} + 6 * \frac{1}{2} \tau_{FA} = 6 \tau_{FA}$ — Optimal
- 4 * 4 * 4 * 4 * 5 M — $5 \tau_{FA} + 2 * \frac{1}{2} \tau_{FA} = 6 \tau_{FA}$ — Optimal
- 5 * 5 * 5 * 6 M — $6 \tau_{FA} + \frac{1}{2} \tau_{FA} = 6 \frac{1}{2} \tau_{FA}$
- 3 * 6 * 6 * 6 M — $6 \tau_{FA} + 3 * \frac{1}{2} \tau_{FA} = 7 \frac{1}{2} \tau_{FA}$



Delay = $3 \tau_{FA} + 6 * \frac{1}{2} \tau_{FA} = 6 \tau_{FA}$
 Area = $3 * 13 A_{FA} + (6 * 3 + 6) A_{MUX}$

→ Manchester Carry

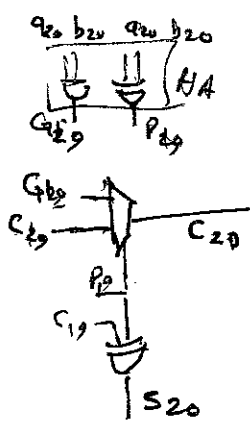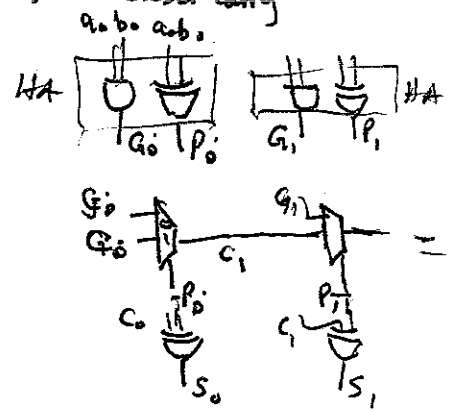

Delay = $\tau_{HA} + 2\phi \tau_{MUX} + \tau_{XOR}$
 Area = $21 A_{HA} + 2\phi A_{MUX} + 2\phi A_{MUX}$

Area wise Manchester carry outperforms carry select Adder
 Speed wise Carry select Adder outperform Manchester carry Adder